

Building circuits to do math


Toki Nishikawa

September 20 2022
6-8pm Tuesday lab with Kim Nguyen/Nick Boudreau

1 Design

The objective of this lab is to construct a circuit that compares two 2-bit numbers. The first step is to create a logic equation which can be done using a truth table and its corresponding Karnaugh map as seen in **Figure 1**. M and N are each 2-bit numbers where M_1, M_0, N_1 and N_0 are the variables associated with the individual bits. M_1 and N_1 are the most significant bits. **Figure 1** shows that the logic equation corresponding to $M > N$ is

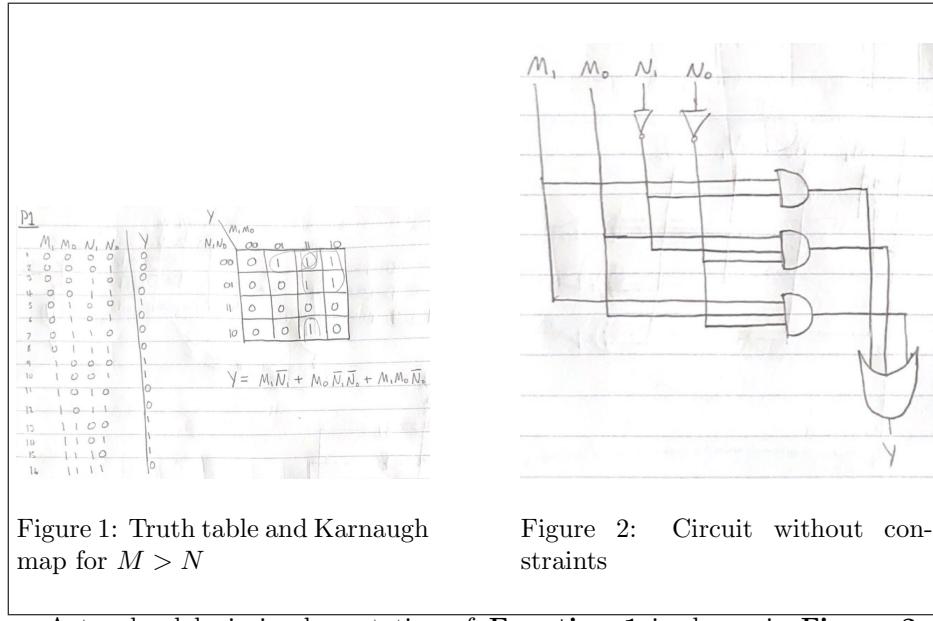
$$Y = M_1 \bar{N}_1 + M_0 \bar{N}_1 \bar{N}_0 + M_1 M_0 \bar{N}_0 \quad (1)$$



A two-level logic implementation of **Equation 1** is shown in **Figure 2**. However, we will construct our circuit under the constraint that we only have access to the following chips:

- 74HC00 quad NAND
- 74HC04 hex inverter
- 74HC4075 3x3 OR
- 74HC266 quad XNOR

Thus, the circuit we will create is the one shown in **Figure 3**. This circuit will only use one 74HC00 quad NAND, one 74HC04 hex inverter, and one 74HC4075 3x3 OR. In order to control the voltages of our inputs (M_1 , M_0 , N_1 and N_0), we will use a DIP switch and pull-up resistors. An open switch will cause current to flow from V_{cc} to the desired input pin whereas a closed switch will cause current to flow straight to ground. The output of our circuit will be connected to an LED so that a lit LED indicates a true output. The schematic of the DIP switch and LED implementation are shown in **Figure 4**.

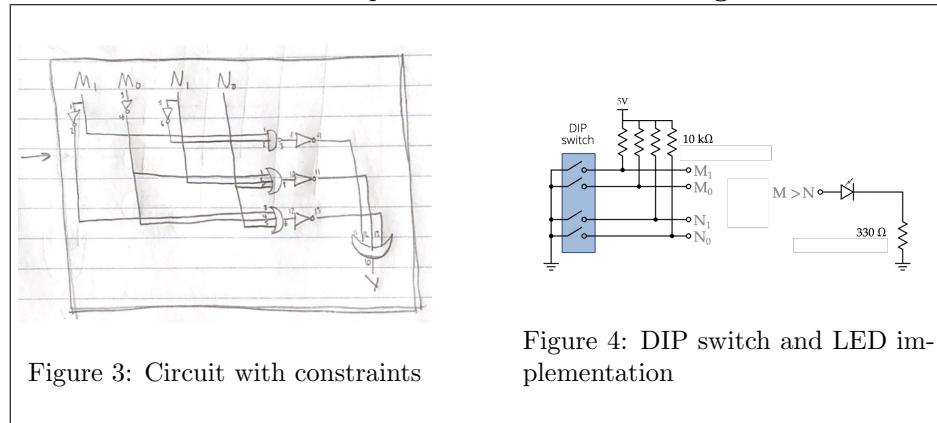

2 Testing

The final circuit is shown in **Figure 5**. It's pretty gross. In order to test its functionality, I tried all 16 combinations of the input variables. These combinations are shown in the truth table in **Figure 1**. The circuit obtained the correct outputs for all of the combinations, and so I'm confident that the implementation is correct.


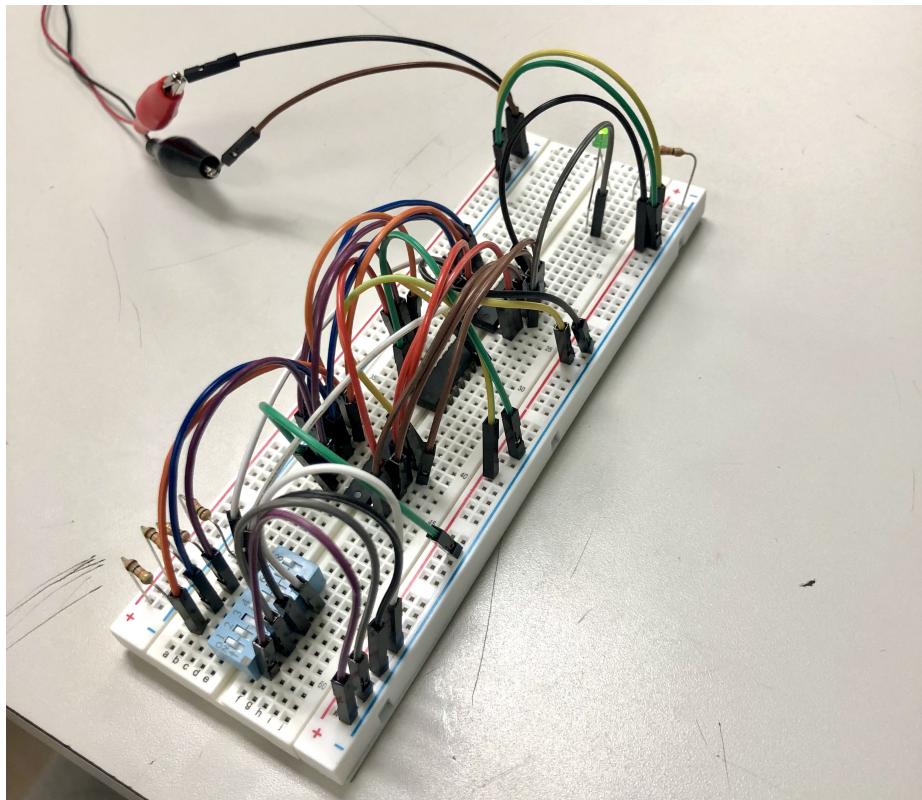


Figure 5: Final circuit on breadboard

3 Lab Journal

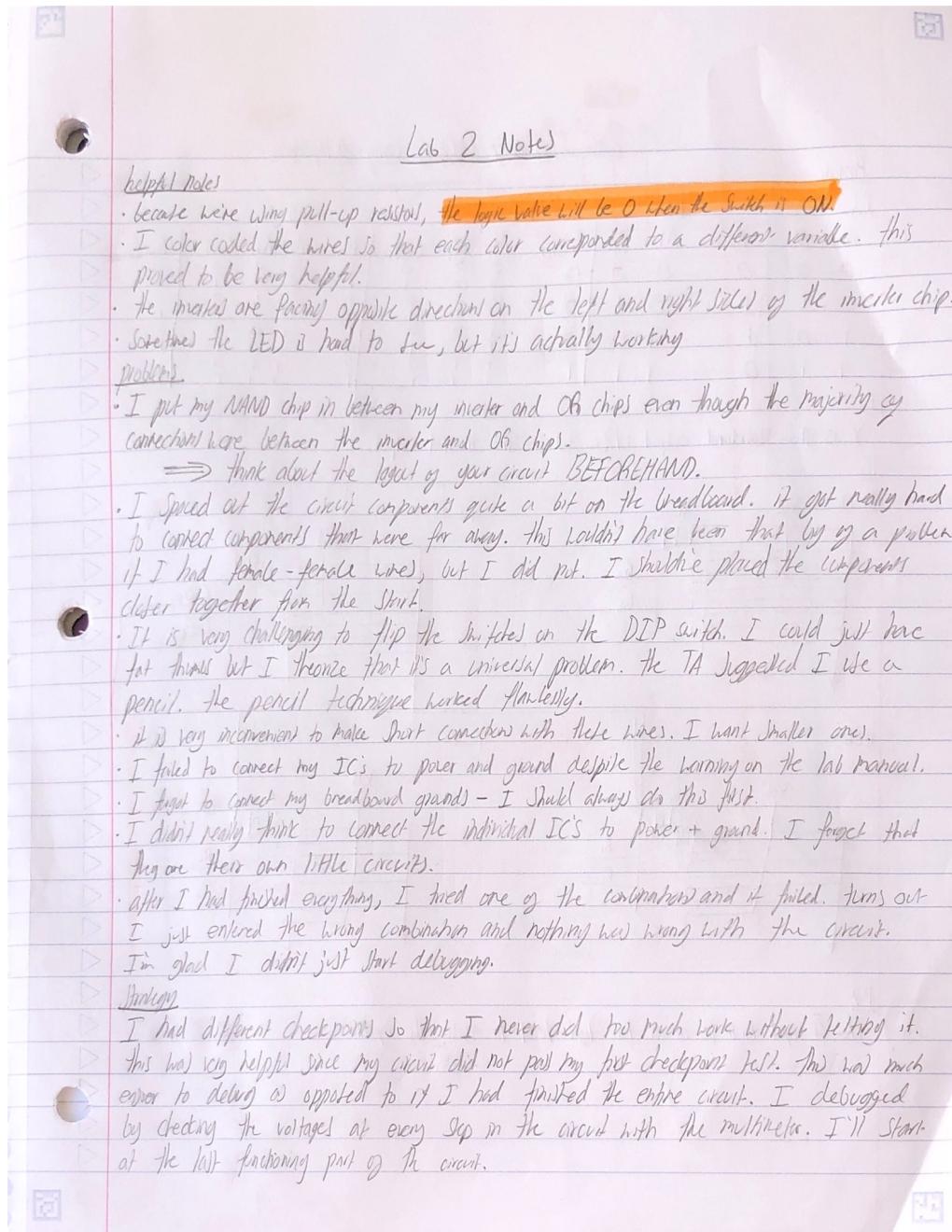

4 Reflection

This was my first experience with designing a circuit that implements a logic equation. It is important to understand the translation from logic to a hardware implementation. Sometimes it's difficult to imagine how hardware could represent even the simplest ideas.

I ran into various issues during this project. One of the most frustrating being the layout of the breadboard. When there are many different logic gate ICs, it becomes difficult to make all the necessary connections between circuit elements. It is especially difficult to make these connections when you don't plan the setup of your ICs beforehand. For example, the IC in the middle of the breadboard shown in **Figure 5** is the NAND gate. It may be difficult to see, but there are hardly any connections associated with this gate. The majority of the connections were between the inverter and the OR gate. It would have been a lot more convenient to have these two gates placed next to each other. In future projects, I plan to consider the connections I'll be making between ICs before I begin building the circuit.

I was able to complete the circuit board in around two hours. With that said, it can definitely be done quicker if you don't make as many mistakes as I did.